

DSM LAB REPORT-6

Group 14: Aaryan Nakul Shah (2024113014)

Lab 6: Latches,
Flip-flops and
Counters

Experiment-1



Objective:

To assemble and test an SR-Latch using its NOR implementation

Components Used:

Digital Test Kit, CD4001 IC and wires

Reference Circuit:

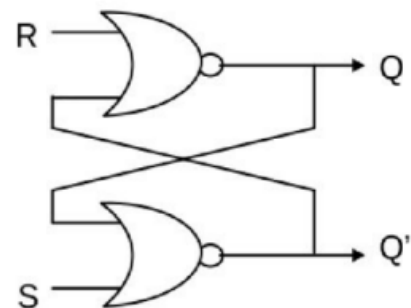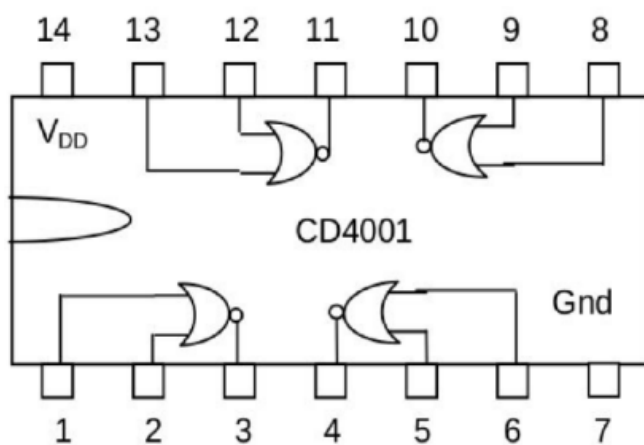


Procedure:



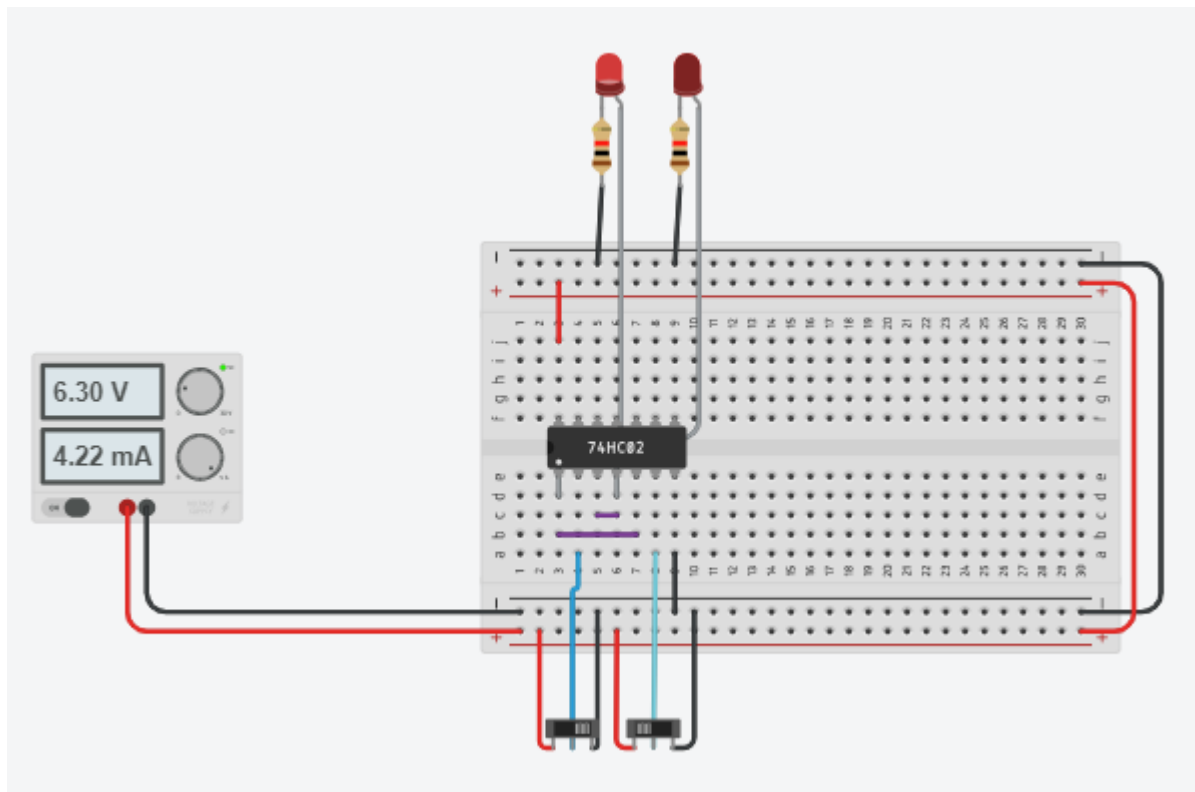
1. Connect the VCC and GND of the Digital Test Kit to the VCC and GND pins of the IC.
2. Using two gates of the IC make connections so as to make a circuit as shown above.

Tinkercad Simulation:

https://www.tinkercad.com/things/iIG49lsVEGX-dsmlab6exp1?sharecode=iGSU0PW0EAgvCBub7nUA2EfoxSnC2XQLFpXK_Xu_33o



Outputs:

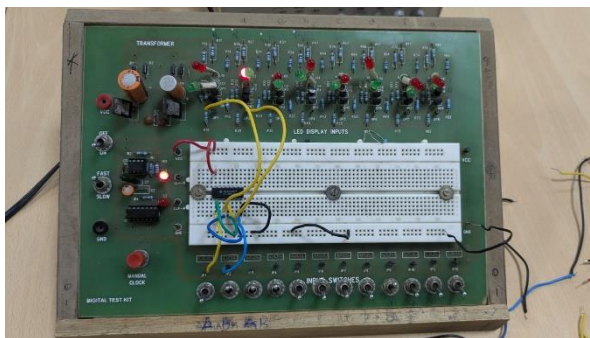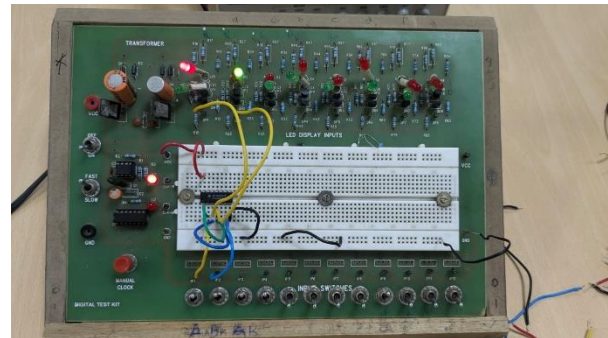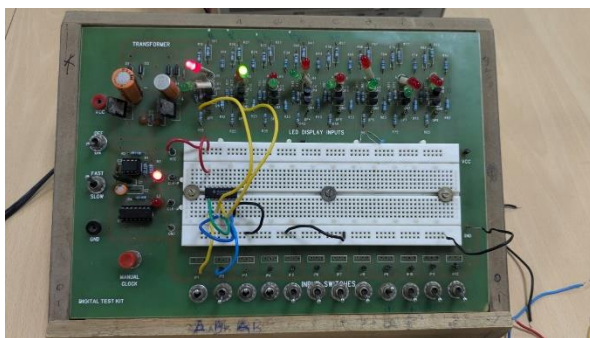

Observations:

S	R	Q	Q'	Action
0	1	0	1	RESET
1	0	1	0	SET
0	0	UNPREDICTABLE		HOLD
1	1	0	0	FORBIDDEN

Conclusion:

NOR-implementation of SR-Latch assembled and tested.

Experiment-2


Objective:

To assemble and test a JK Master-Slave Flip Flop

Components Used:

Digital Test Kit, ICs = CD4012, CD4001 and wires

Reference Circuit:

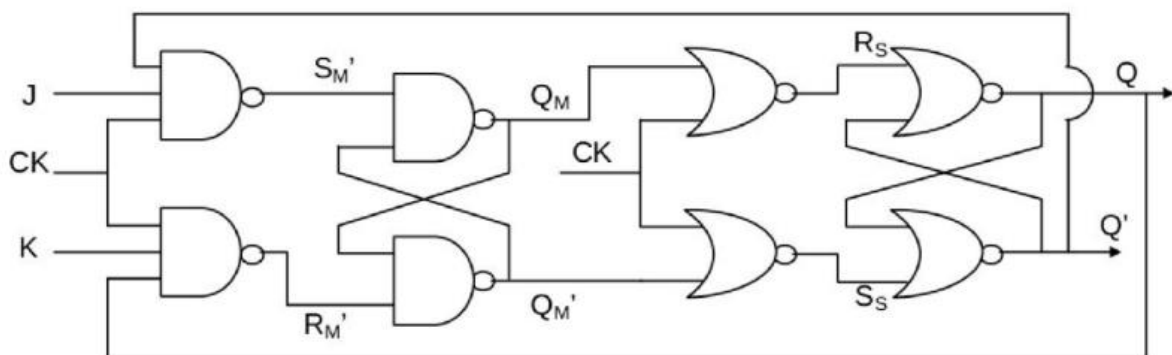


Procedure:

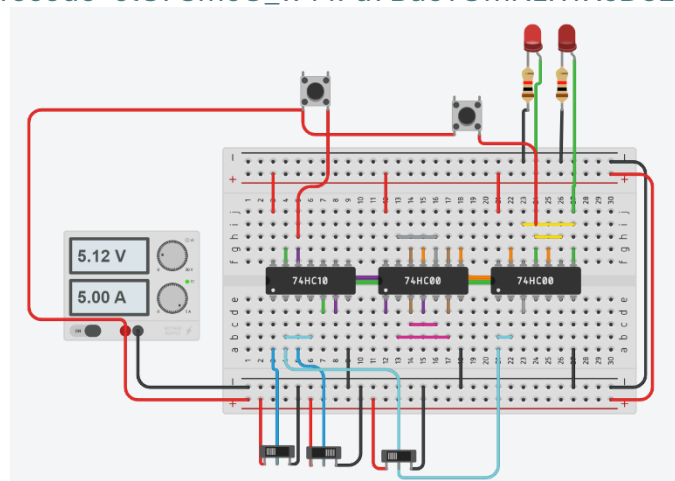1. Connect the VCC and GND of the Digital Test Kit to the VCC and GND pins of the ICs.
2. Make connections as shown above to form the necessary circuit.

Tinkercad Simulation:

https://www.tinkercad.com/things/iqd6yzODoqe-dsmlab6exp2?sharecode=9lOFSm6O_w44Pu7BucYOmNzR1X6D8LovoZX2b5hBFV4



Output:

JK Master-Slave Flip Flop.mp4

Observations:

clk	J	K	Q(t+1)
0	X	X	Q(t)
1	0	0	Q(t)
1	0	1	0
1	1	0	1
1	1	1	Q'(t)

Conclusion:

JK Master Slave Flip Flop assembled and tested.

Experiment 3:

Objective:

Using an Arduino to implement a 4-bit up-down ripple counter.

Components Used:


Digital Test Kit, Arduino Uno board and wires

Procedure:

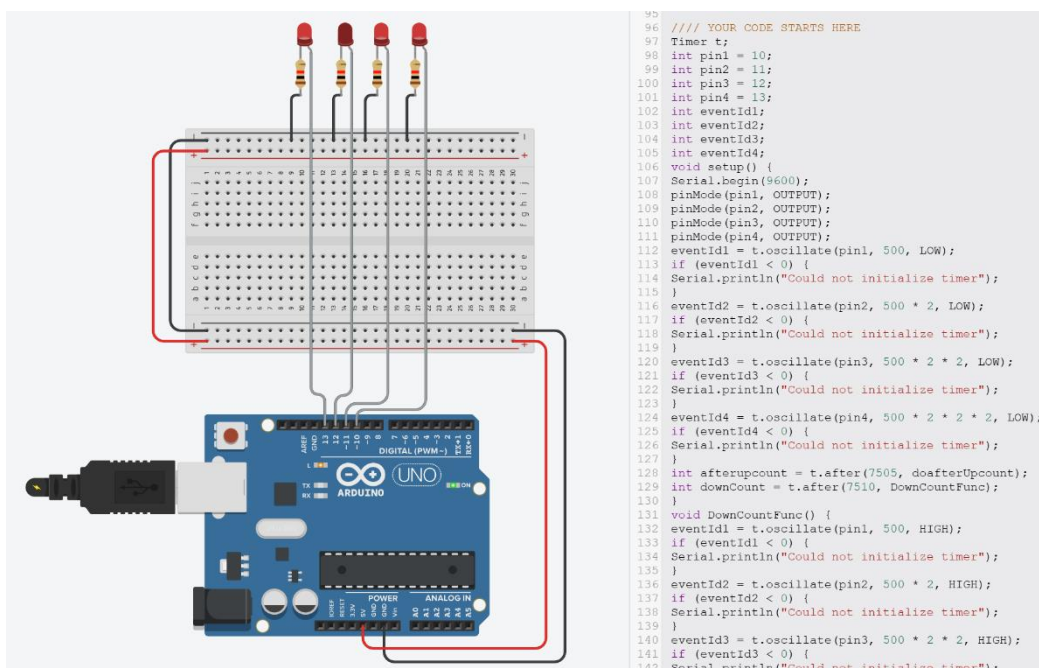1. Connect the VCC and GND of the Digital Test Kit to the VCC and GND of the Arduino.
2. Connect the Digital Pins of the Arduino to the Display Points of the Digital Test Kit.
3. Write the appropriate code for the up-down counter.

Tinkercad Simulations:

<https://www.tinkercad.com/things/4Tkq9BMEozE-dsmlab6exp3?sharecode=huGLRJGLYVb3NPWgBkdN7uYk99QgpbMvQRv4S2gGLXA>



```

96  ///// YOUR CODE STARTS HERE
97  Timer t;
98  int pin1 = 10;
99  int pin2 = 11;
100 int pin3 = 12;
101 int pin4 = 13;
102 int eventId1;
103 int eventId2;
104 int eventId3;
105 int eventId4;
106 void setup() {
107   Serial.begin(9600);
108   pinMode(pin1, OUTPUT);
109   pinMode(pin2, OUTPUT);
110   pinMode(pin3, OUTPUT);
111   pinMode(pin4, OUTPUT);
112   eventId1 = t.oscillate(pin1, 500, LOW);
113   if (eventId1 < 0) {
114     Serial.println("Could not initialize timer");
115   }
116   eventId2 = t.oscillate(pin2, 500 * 2, LOW);
117   if (eventId2 < 0) {
118     Serial.println("Could not initialize timer");
119   }
120   eventId3 = t.oscillate(pin3, 500 * 2 * 2, LOW);
121   if (eventId3 < 0) {
122     Serial.println("Could not initialize timer");
123   }
124   eventId4 = t.oscillate(pin4, 500 * 2 * 2 * 2, LOW);
125   if (eventId4 < 0) {
126     Serial.println("Could not initialize timer");
127   }
128   int afterupcount = t.after(7505, doafterUpcount);
129   int downCount = t.after(7510, DownCountFunc);
130   }
131   void DownCountFunc() {
132     eventId1 = t.oscillate(pin1, 500, HIGH);
133     if (eventId1 < 0) {
134       Serial.println("Could not initialize timer");
135     }
136     eventId2 = t.oscillate(pin2, 500 * 2, HIGH);
137     if (eventId2 < 0) {
138       Serial.println("Could not initialize timer");
139     }
140     eventId3 = t.oscillate(pin3, 500 * 2 * 2, HIGH);
141     if (eventId3 < 0) {
142       Serial.println("Could not initialize timer");
143     }
144     eventId4 = t.oscillate(pin4, 500 * 2 * 2 * 2, HIGH);
145     if (eventId4 < 0) {
146       Serial.println("Could not initialize timer");
147     }
148     int afterupcount = t.after(7505, doafterUpcount);
149   }
150   void doafterUpcount() {
151     t.stop(eventId1);
152     t.stop(eventId2);
153     t.stop(eventId3);
154     t.stop(eventId4);
155   }
156   void loop() {
157     t.update();
158   }
159   void stopAllTimers() {
160   }
161  ///// YOUR CODE ENDS HERE

```


Observations:

The counter displays the numbers 0 to 15 in binary using LEDs. In this representation, a HIGH output of the LED indicates a 1, while a LOW output represents a 0. After reaching 15, the counter begins displaying numbers in reverse order.

Conclusion:

4-bit up-down ripple counter successfully assembled using an Arduino.